

* Sample - And - Hold: amplitude.

- TO convert this signal into digital form, we have two ways.

 


Fig: A time-varying Analog signal $v(t) = V \sin \omega t$

- ① The value of the signal at every instant of time is required to be converted into a group of 'n' no. of bits.
 - This process will yield an infinite no. of analog voltage values & thus is not at all practicable
- ② TO take samples of $v(t)$ at regular intervals, i.e.; signal is sampled regularly every T_s .
 - Then according to sampling theorem, the signal can be uniquely determined & reconstructed from these samples with no error
 - Time $T_s \rightarrow$ sampling time & $f_s = \frac{1}{T_s}$ sampling rate
 - According to sampling theorem, $f_s \geq 2f$ where $f \rightarrow$ frequency of the analog signal.

- The constant voltage corresponding to each sample is obtained using a sample-and-hold (S/H) circuit
- The o/p of the S/H circuit is converted to digital signal by means of an analog-to-digital (A/D) converter circuit-

Sample-and-Hold Circuit:

- In this circuit, voltage across the capacitor follows the i/p signal voltage $V_i \rightarrow$ when S is closed.

 


Fig: Basic sample-and-hold circuit

Sample and Hold ckt samples the i/p signal and holds on to its last sampled value until the i/p is sampled again.

- When S is open $\rightarrow$ capacitor holds the instantaneous value of the signal voltage attained just before S is opened.
- Thus for every T_s , switch is closed for a short duration & then opened.

- The dc voltage across the capacitor gives the value of the signal at the instant the switch is opened
- The dc voltage represents a sample of the signal E_i is converted to digital signal using A/D converter ckt

 



Fig: A practical sample-and-hold circuit

- Fig consists of two ^{units} gain amplifiers A_1 and A_2 and a digitally controlled switch S .
- Analog i/p voltage is applied at the i/p of buffer amplifier A_1 .
- These (op-Amps) have high i/p impedances & low o/p impedances.
- The high i/p impedance of A_1 will prevent loading of the analog signal & its low o/p imp. will help in fast charging of the capacitor when S is closed.

- Switch is controlled by a clock generator which makes the switch operate at regular intervals as required according to the sampling rate -
- The voltage across the capacitor is applied at the i/p of the analog-to-digital converter through buffer amplifier A_2 .
- Here, the high i/p imp. of A_2 avoids discharge of capacitor due to loading effect of A/D converter.
- Accuracy of the ckt depends upon the holding of the charge in the capacitor.
- Therefore, a capacitor with a very low leakage must be used.
- A capacitor with polycarbonate, polyethylene or Teflon dielectric is preferred.

* Functional diagram of ADC:
 or

Schematic of ADC

 


- It accepts an analog i/p voltage V_a & produces an o/p binary word $d_1, d_2, \dots, d_n$ of functional value D , so that

$$D = d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n}$$

where $d_1 \rightarrow \text{MSB}$; $d_n \rightarrow \text{LSB}$.

- An ADC usually has two additional control lines :
 - $\rightarrow \text{START} \rightarrow$ i/p to tell ADC when to start conversion
 - $\rightarrow \text{EOC} \rightarrow$ o/p to tell when to end conversion
- Depending upon type of application, ADCs are designed for microprocessor interfacing or ^{to} directly drive LCD or LED displays.

Types of ADCs:

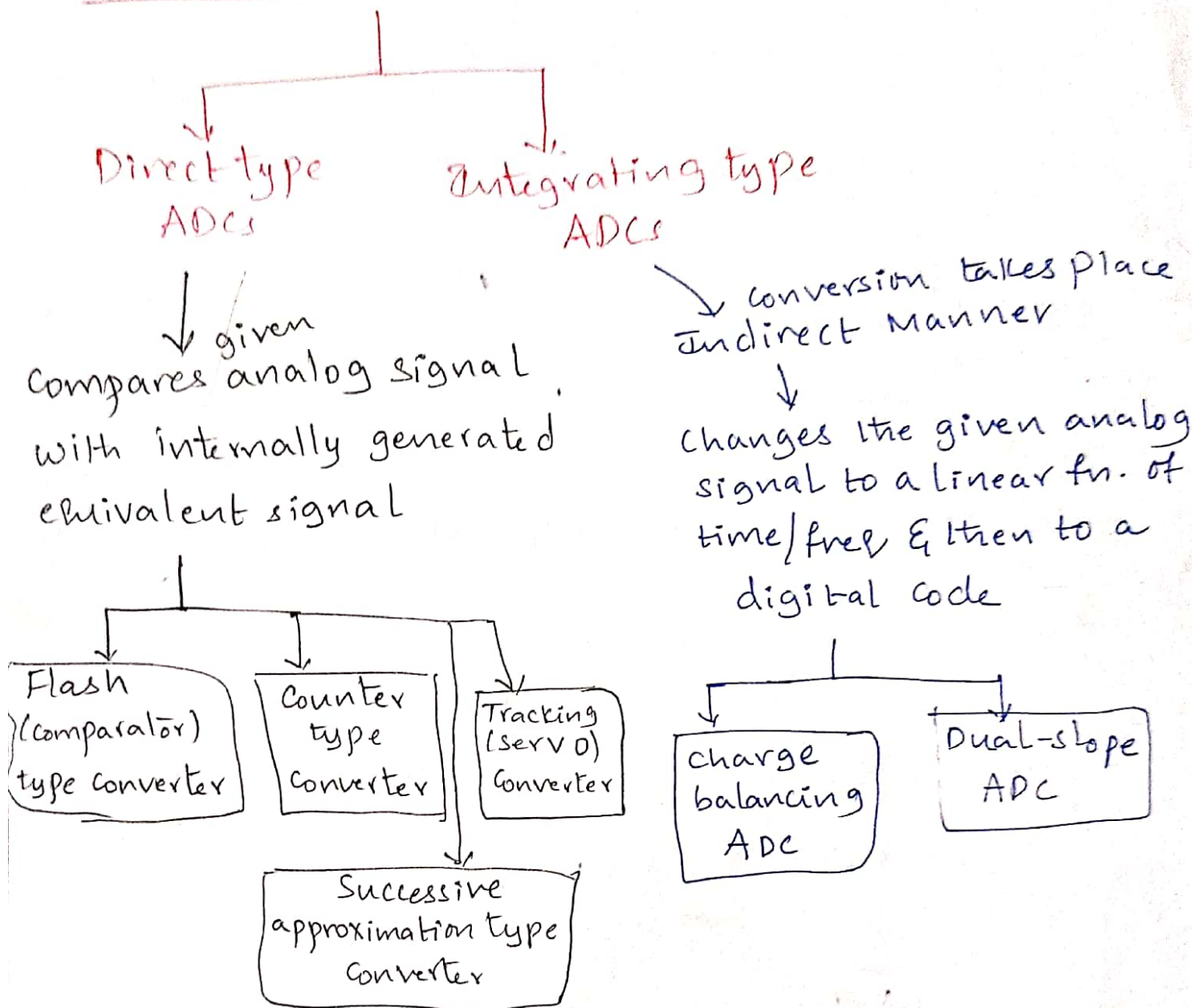

— Most commonly used ADCs are Successive approximation and the integrator type

* Quantization and Encoding:

- In D/A converter, possible no. of digital i/p is fixed.
Ex: In a 3-bit D/A converter, there are 8 possible i/p.
- In contrast, the in A/D converter, the i/p analog voltage can have any value in a range, but the digital o/p can have only 2^N discrete values for n -bit A/D converter.
- Therefore, the whole range of analog voltage is required to be represented suitably in 2^N intervals. This process is known as Quantization.
- Each interval is then assigned a unique N -bit binary code, which is referred to as encoding.

Example: Consider an analog voltage in the range of 0 to V and a 3-bit digital o/p for any in the range

↳ let's divide whole range in 8 intervals with size $s = V/8$.

↳ Each interval is assigned a 3-bit binary Value

Analog Voltage

Equivalent digital value.

V	_____	111
$7/8 V$	_____	110
$6/8 V$	_____	101
$5/8 V$	_____	100
$4/8 V$	_____	011
$3/8 V$	_____	010
$2/8 V$	_____	001
$1/8 V$	_____	000
0	_____	

Fig: Quantization & Encoding

→ We can observe that the whole range of voltage in an interval is represented by only one digital value

→ i.e) if ^{given} V voltage is in the range 0 to $1/8 V$, 000 will be the represented digital value

↳ This leads to the error in the Conversion process, which is called Quantization error

→ Quantization error can be reduced if the size of

$\begin{cases} \rightarrow \text{top \& bottom intervals as } s/2 \\ \rightarrow \text{middle six intervals as } s \end{cases}$ is assumed

→ Quantization error can also be specified in terms of LSB.

↳ Max. quantization error is $\pm \frac{1}{2} \text{ LSB}$.

* Parallel-comparator A/D converter:

- Also called as Flash A/D Converter
- Simplest, possible A/D converter
fastest
- Expensive technique
- Fig shows a 3-bit A/D Converter

Fig Description: circuit comprises of

- a resistive divider n/w
- 7 op-amp comparators
- latches
- Decoder
- i/p to the ckt is $V_a \rightarrow$ Analog voltage
- $V \rightarrow$ Reference voltage
↳ Full scale voltage

Working:

— At each node of the resistive divider, a comparison voltage is available

 


Fig. 10.19, Table 10.6

Advantage of this ADC (A/D Converter),

- ↳ provides high speed conversion; fastest
- ↳ conversion time is 100ns or less.

Disadvantage of this ADC (A/D Converter):

- ↳ No. of comparators approximately doubles for each added bit
- ↳ In general, for n-bit converter $(2^n - 1)$ comparators are required

Ex: A 2-bit ADC requires 3 comparators.

3 u u 7 4
4 u u 15 u